

## 6

## CHAPTER


# Alternating Currents

## JEE/NEET Syllabus

Alternating currents, peak and rms value of alternating current/ voltage; reactance and impedance; LCR series circuit, resonance; Quality factor, power in AC circuits, wattless current
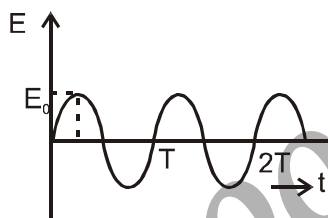
### ALTERNATING CURRENT

A time varying, periodic current is called an ac when its amplitude is constant and alternate half cycles are positive and negative.



The alternating emf  $E$  at any instant may be expressed as  $E = E_0 \sin \omega t$  where  $\omega$  is angular frequency of alternating emf and  $E_0$  is the peak value or amplitude of alternating emf.

The frequency of alternating emf,  $f = \omega/2\pi$  and time period of alternating emf.,  $T = 1/f = 2\pi/\omega$ .

The alternating current in a circuit, fed by an alternating source of emf may be controlled by inductance  $L$ , resistance  $R$  and capacitance  $C$ . Due to presence of elements  $L$  and  $C$ , the current is not necessarily in phase with the applied emf. Therefore alternating current is, in general expressed as  $I = I_0 \sin(\omega t + \phi)$  where  $\phi$  is the phase which may be positive, zero or negative depending on the value of reactive components  $L$  and  $C$ .

### AVERAGE AND RMS VALUE OF AC

#### 1. Mean or Average value for time 't'

$$E_{\text{mean}} = \frac{1}{t} \int_0^t E dt, \quad I_{\text{mean}} = \frac{1}{t} \int_0^t I dt$$

#### 2. Root Mean Square (RMS) Value

RMS value of ac is equal to that value of dc, which when passed through a resistance for a given time will produce the same amount of heat as produced by the ac when passed through the same resistance for same time.

RMS values are also known as **virtual or effective value**.

### THIS CHAPTER COVERS :

- Alternating current
- Average and rms value of AC
- Phasors and component of AC circuit
- Series LCR circuit
- Power consumed in AC circuit

Cases :

$$E_{\text{rms}}^2 = \frac{1}{T} \int_0^T E^2 dt, \quad I_{\text{rms}}^2 = \frac{1}{T} \int_0^T I^2 dt$$

1.  $I_{\text{mean}} = 0$  for  $t = T$

$$I_{\text{mean}} = \frac{2I_0}{\pi} \text{ for } t = T/2$$

$$I_{\text{rms}} = \frac{I_0}{\sqrt{2}} \text{ for } t = T$$

$$I_{\text{rms}} = \frac{I_0}{\sqrt{2}} \text{ for } t = T/2$$

2.  $I_{\text{mean}} = \frac{I_0}{\pi} t = T$

$$I_{\text{mean}} = \frac{2I_0}{\pi} t = T/2$$

$$I_{\text{rms}} = \frac{I_0}{2} \text{ for } t = T$$

$$I_{\text{rms}} = \frac{I_0}{\sqrt{2}} \text{ for } t = T/2$$

3.  $I_{\text{mean}} = \frac{2I_0}{\pi}$  for  $t = T$

$$I_{\text{mean}} = \frac{2I_0}{\pi}$$
 for  $t = T/2$

$$I_{\text{rms}} = \frac{I_0}{\sqrt{2}}$$
 for  $t = T$


$$I_{\text{rms}} = \frac{I_0}{\sqrt{2}}$$
 for  $t = T/2$

4.  $I_{\text{mean}} = 0$  for  $t = T$


$$I_{\text{mean}} = I_0$$
 for  $t = T/2$

$$I_{\text{rms}} = I_0$$
 for  $t = T$


$$I_{\text{rms}} = I_0$$
 for  $t = T/2$

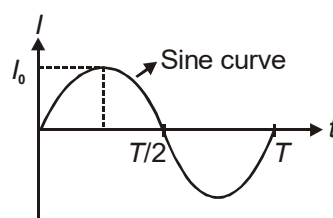


Case-1

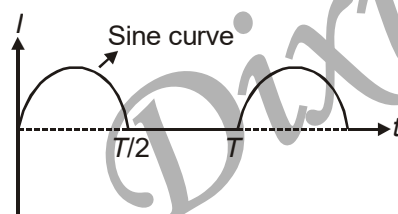

Case-2

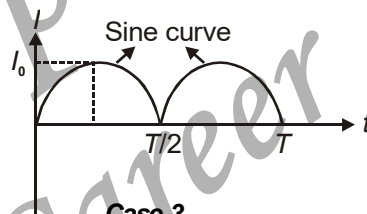

Case-3


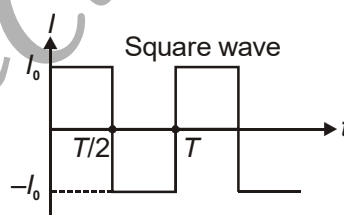


Case-4

## PHASOR AND AC CIRCUITS

### Phasor

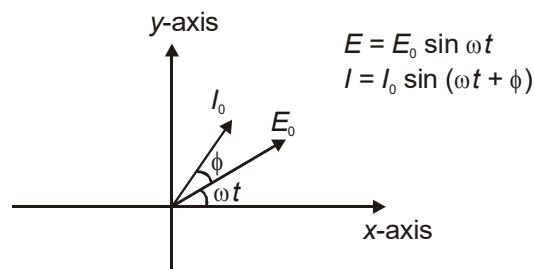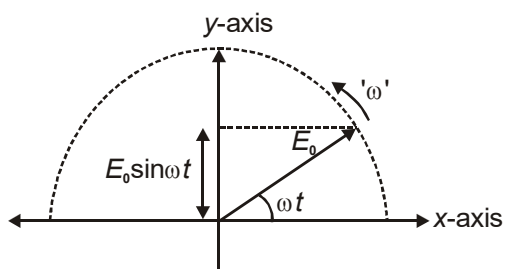1. A vector rotating in anticlockwise direction with angular velocity ' $\omega$ '.



2. Its length is equal to amplitude of alternating quantity.
3. Projection of vector on y-axis gives the instantaneous value of alternating quantity.

## Different ac Circuits

### 1. Resistive Circuit

$$I = I_0 \sin \omega t$$

$$I_0 = \frac{E_0}{R}$$

### 2. Inductive Circuit

$$I = I_0 \sin (\omega t - \pi/2)$$

$$I_0 = \frac{E_0}{X_L}, \text{ where } X_L = \omega L = 2\pi fL$$

### Capacitive Circuit

$$1. I = I_0 \sin (\omega t + \pi/2)$$

$$2. I_0 = \frac{E_0}{X_C}, \text{ where } X_C = \frac{1}{\omega C} = \frac{1}{2\pi vC}$$

## SERIES LCR CIRCUIT

$$V = \frac{E_0}{\sqrt{2}} = \text{rms value of applied voltage}$$

$$V_L = \text{rms voltage across } L = V_L - V_C$$

$$V_R = \text{rms voltage across } R = V_R$$

### Phase Relationship

$I$  and  $V_R$  are in same phase.

$V_L$  leads  $I$  by  $90^\circ$ .

$V_C$  lags behind  $I$  by  $90^\circ$ .

#### Case 1 :

$$V_L > V_C$$

$\Rightarrow V$  leads  $I$  by  $\phi$

$$\text{where } \tan \phi = \frac{V_L - V_C}{V_R}$$

$$\tan \phi = \frac{X_L - X_C}{R}$$

$$\text{Here } X_L > X_C \text{ i.e., } \omega > \frac{1}{\sqrt{LC}}$$






#### Case 2 :

$$V_L < V_C$$


i.e.,  $V$  lags behind  $I$  by  $\phi$

$$\tan \phi = \frac{V_C - V_L}{V_R} = \frac{X_C - X_L}{R}$$
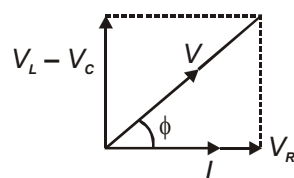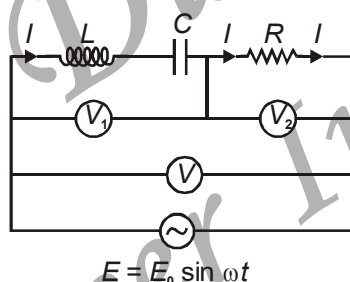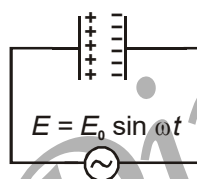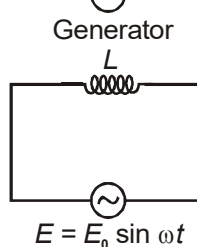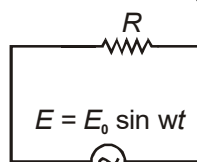
$$\text{Here } X_C > X_L \text{ i.e., } \omega < \frac{1}{\sqrt{LC}}$$



Phasor diagram

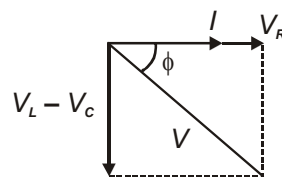

Phasor diagram

In both cases  $V = \sqrt{V_R^2 + (V_L - V_C)^2} = I\sqrt{R^2 + (X_L - X_C)^2}$

(a) Impedance =  $Z = \sqrt{R^2 + (X_L - X_C)^2}$

(b) Power factor =  $\cos \phi = \frac{R}{Z} = \frac{R}{\sqrt{R^2 + (X_L - X_C)^2}}$

**Case 3 :**

$V_L = V_C$  i.e.,  $X_L = X_C$  i.e.,  $\omega = \frac{1}{\sqrt{LC}}$  [Resonance]

In this case

(a)  $V_2 = V = \frac{E_0}{\sqrt{2}}$

(b)  $V_1 = V_L - V_C = 0$



(c)  $\tan \phi = 0$ , or  $\phi = 0$

(d)  $\cos \phi = 1$

(e)  $Z = R$  (minimum)

(f) Power consumed is maximum

(g) Graphs :

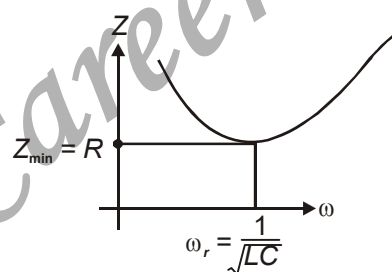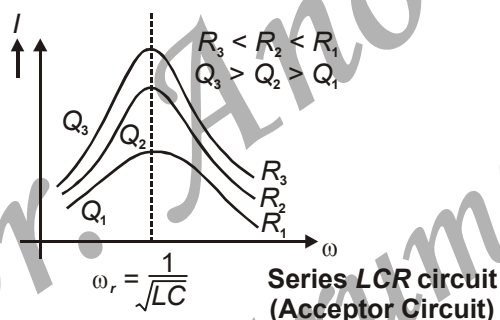

(h) In a series LCR circuit,

(i) When voltage leads current, then to bring resonance state, either  $L$  or  $C$  should be decreased.

(ii) If voltage lags behind current, then to bring resonance state either  $L$  or  $C$  should be increased.


(iii) Quality factor  $Q$  represents the sharpness of tuning at resonance

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}} \quad \text{i.e.,} \quad Q \propto \frac{1}{R}$$

**Case 4 : Series LR Circuit**


(a)  $Z = \sqrt{R^2 + X_L^2}$ ,  $V = \sqrt{V_R^2 + V_L^2}$ ,  $I = \frac{V}{Z}$

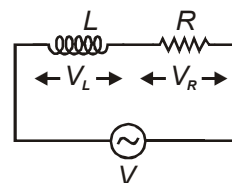(b)  $\cos \phi = \frac{R}{\sqrt{R^2 + X_L^2}}$ ,  $\tan \phi = \frac{X_L}{R}$ . Voltage leads current



$$(a) \quad V = \sqrt{V_R^2 + V_C^2}, \quad Z = \sqrt{R^2 + X_C^2}, \quad I = \frac{V}{Z}$$

$$(b) \quad \cos \phi = \frac{R}{Z} = \frac{R}{\sqrt{R^2 + X_C^2}}, \quad \tan \phi = \frac{X_C}{R}. \text{ Voltage lags behind current}$$

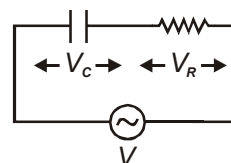



**Case 6 : Series LC Circuit**

$$(a) \quad V = V_L - V_C, \quad Z = X_L - X_C, \quad I = \frac{V}{Z}$$

$$(b) \quad \phi = \frac{\pi}{2} (X_L > X_C), \quad \phi = \frac{-\pi}{2} (X_L < X_C)$$

$$(c) \quad \text{When } X_L = X_C, \quad Z = 0$$
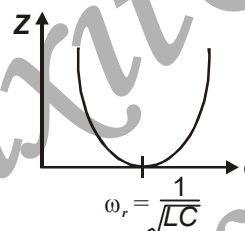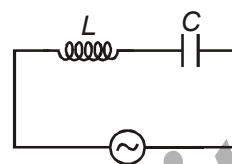
$$\text{i.e., } \omega = \frac{1}{\sqrt{LC}}$$



**POWER CONSUMED IN AN A.C. CIRCUIT**

$$P_{av} = \frac{1}{T} \int_0^T E i dt$$

If  $E = E_0 \sin \omega t$  and  $i = I_0 \sin (\omega t + \phi)$

$$P_{av} = \frac{E_0 I_0}{2} \cos \phi = \frac{E_0}{\sqrt{2}} \cdot \frac{I_0}{\sqrt{2}} \cos \phi = E_v I_v \cos \phi$$

[ $E_v$  = Virtual or rms voltage,  $I_v$  = Virtual or rms current]

**Some Important Points :**

1. For pure resistor  $\phi = 0$ ,  $P_{av} = \frac{E_0 I_0}{2} = E_{rms} I_{rms}$
2. For pure inductor or capacitor,  $P_{av} = 0$  [Non **resistive** circuit]
3. Power consumed is independent of  $I_v \sin \phi$ . This is called wattless component.
4.  $\cos \phi$  = Power factor =  $\frac{R}{Z}$
5. In a series LCR circuit

$$P_{av} = E_v I_v \cos \phi = \frac{E_v^2}{Z} \cos \phi = I_v^2 R$$

Wattless current  $I_v \sin \phi$

6. At resonance i.e., at  $\omega_r = \frac{1}{\sqrt{LC}}$ ,  $Z = R$  power is maximum

7. At frequencies other than  $\omega_r = \frac{1}{\sqrt{LC}}$ , power consumed is less.

8. At  $\omega = \omega_1$  or  $\omega_2$ , power = half the maximum power then  $\omega_r = \sqrt{\omega_1 \omega_2}$

$$P_{\max} = I_{\max}^2 R$$

$$P_{1/2} = \frac{I_{\max}^2 R}{2} = \left( \frac{I_{\max}}{\sqrt{2}} \right)^2 R$$

i.e., when  $I = \frac{I_{\max}}{\sqrt{2}}$ , power is half

$$I_{\max} = \frac{E_v}{R}, I_v = \frac{E_v}{Z}$$

$$I = \frac{I_{\max}}{\sqrt{2}} \Rightarrow \boxed{Z = R\sqrt{2}}$$

$$\text{or, } \sqrt{(X_L - X_C)^2 + R^2} = R\sqrt{2} \Rightarrow \boxed{X_L - X_C = R}$$

$$\cos \phi = \frac{R}{Z} = \frac{1}{\sqrt{2}} \Rightarrow \phi = 45^\circ$$

9. Quality factor  $Q = \frac{\omega_r}{\omega_2 - \omega_1} = \frac{1}{R} \sqrt{\frac{L}{C}}$

and  $\Delta\omega = \omega_2 - \omega_1 = \frac{R}{L}$

